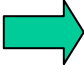



# DIGITAL LOGIC CIRCUITS

**Digital logic circuits**  electronic circuits that handle information encoded in binary form (deal with signals that have only two values, **0** and **1**)

 *Digital* .... computers, watches, controllers, telephones, cameras, ...

## BINARY NUMBER SYSTEM

---

*Number ....in  
whatever base*

*Decimal value of the given number*

---

Decimal:    **1,998**    =  $1 \times 10^3 + 9 \times 10^2 + 9 \times 10^1 + 8 \times 10^0 = 1,000 + 900 + 90 + 8 = \mathbf{1,998}$

Binary:

**11111001110**    =  $1 \times 2^{10} + 1 \times 2^9 + 1 \times 2^8 + 1 \times 2^7 + 1 \times 2^6 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 =$   
 $1,024 + 512 + 258 + 128 + 64 + 8 + 4 + 2 = \mathbf{1,998}$


---

## Powers of 2

$N$	$2^N$	<i>Comments</i>
0	1	
1	2	
2	4	
3	8	
4	16	
5	32	
6	64	
7	128	
8	256	
9	512	
10	1,024	“Kilo” as $2^{10}$ is the closest power of 2 to 1,000 (decimal)
11	2,048	
15	32,768	$2^{15}$ Hz often used as clock crystal frequency in digital watches
20	1,048,576	“Mega” as $2^{20}$ is the closest power of 2 to 1,000,000 (decimal)
30	1,073,741,824	“Giga” as $2^{30}$ is the closest power of 2 to 1,000,000,000 (decimal)

## Negative Powers of 2

$N < 0$	$2^N$
-1	$2^{-1} = 0.5$
-2	$2^{-2} = 0.25$
-3	$2^{-3} = 0.125$
-4	$2^{-4} = 0.0625$
-5	$2^{-5} = 0.03125$
-6	$2^{-6} = 0.015625$
-7	$2^{-7} = 0.0078125$
-8	$2^{-8} = 0.00390625$
-9	$2^{-9} = 0.001953125$
-10	$2^{-10} = 0.0009765625$
...	

 

### Binary numbers less than 1

---

*Binary*


*Decimal value*

---

$$\mathbf{0.101101} = 1 \times 2^{-1} + 1 \times 2^{-3} + 1 \times 2^{-4} + 1 \times 2^{-6} = \mathbf{0.703125}$$

---

# ◆ HEXADECIMAL

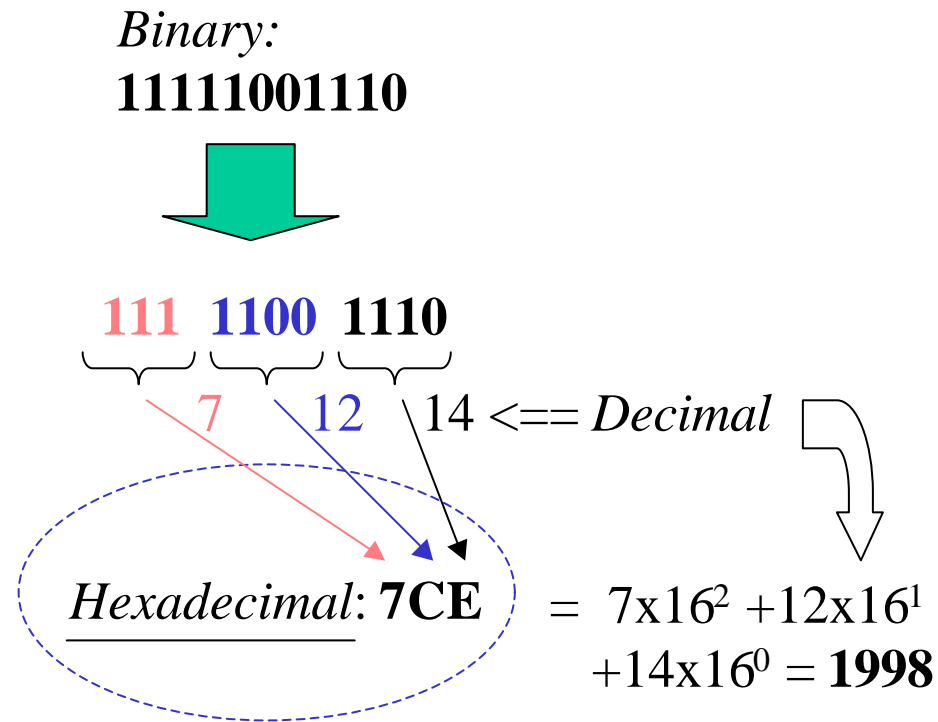

Binary	Decimal	Hexadecimal
0000	0	<b>0</b>
0001	1	<b>1</b>
0010	2	<b>2</b>
0011	3	<b>3</b>
0100	4	<b>4</b>
0101	5	<b>5</b>
0110	6	<b>6</b>
0111	7	<b>7</b>
1000	8	<b>8</b>
1001	9	<b>9</b>
1010	10	<b>A</b>
1011	11	<b>B</b>
1100	12	<b>C</b>
1101	13	<b>D</b>
1110	14	<b>E</b>
1111	15	<b>F</b>

## ★ LOGIC OPERATIONS AND TRUTH TABLES


Digital logic circuits handle data encoded in binary form, i.e. signals that have only two values, **0** and **1**.

- ▶ Binary logic dealing with “true” and “false” comes in handy to describe the behaviour of these circuits: **0** is usually associated with “**false**” and **1** with “**true**.”
- ◆ Quite complex digital logic circuits (e.g. entire computers) can be built using a few *types of basic circuits* called **gates**, each performing a single elementary logic operation : *NOT, AND, OR, NAND, NOR*, etc..
- ▶ Boole’s binary algebra is used as a formal / mathematical tool to describe and design complex binary logic circuits.

 **GATES**


A	$\overline{A}$
0	1
1	0

*NOT*

 


A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

*AND*

 

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

*OR*

 




## ... more GATES


A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

*NAND*

 

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

*NOR*

 




## ... and more GATES


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

*XOR*

 

A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

*EQU* or *XNOR*

 









## GATES ... with more inputs


### EXAMPLES OF GATES WITH THREE INPUTS

A	B	C	$A \cdot B \cdot C$	$A+B+C$	$\overline{A \cdot B \cdot C}$	$\overline{A+B+C}$
0	0	0	0	0	1	1
0	0	1	0	1	1	0
0	1	0	0	1	1	0
0	1	1	0	1	1	0
1	0	0	0	1	1	0
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	0	0

    

★ Logic Gate Array that Produces an Arbitrarily Chosen Output

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

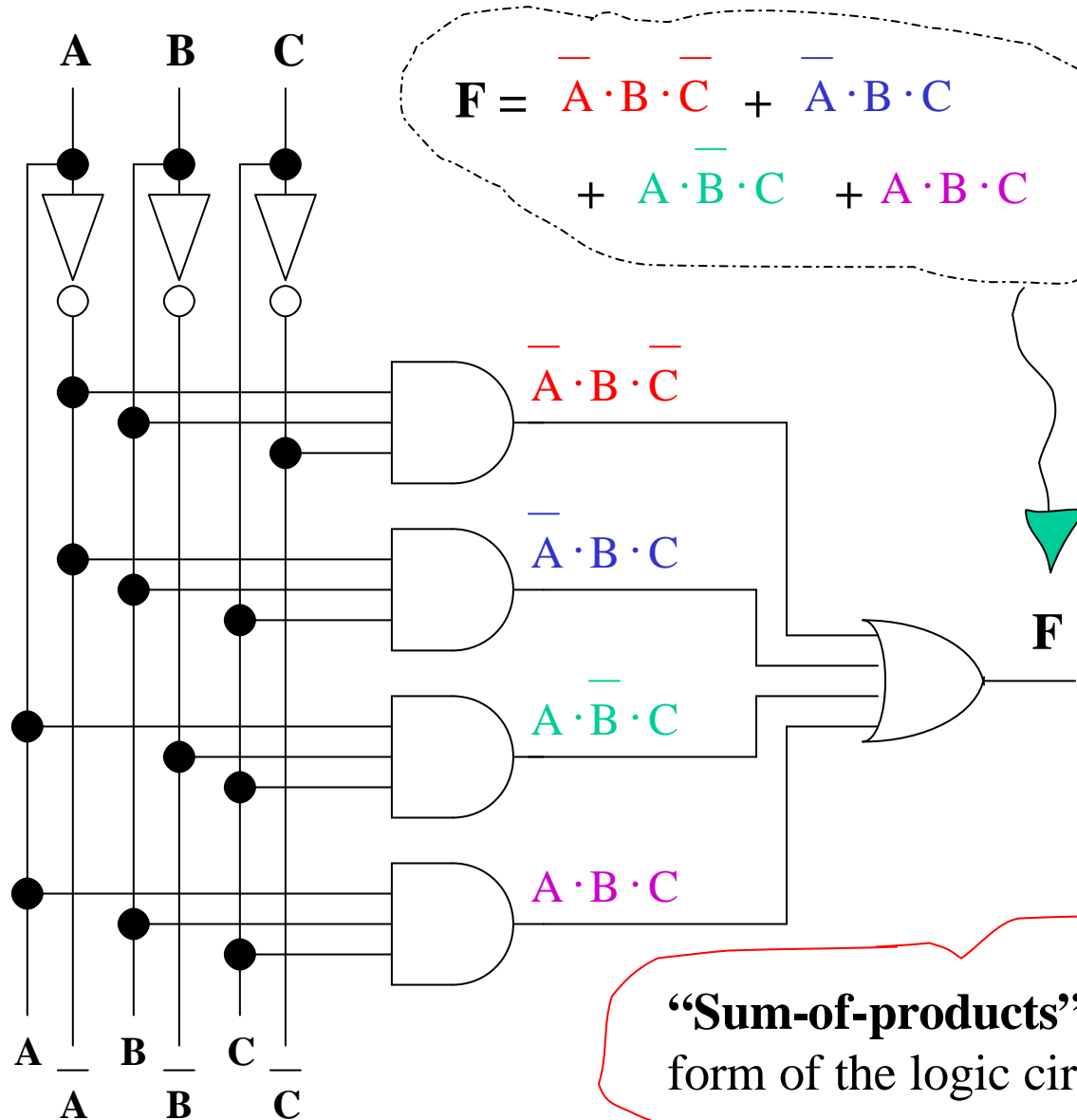



# BOOLEAN ALGEBRA

## AND rules

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

$$0 \cdot A = 0$$

$$1 \cdot A = A$$

$$A \cdot B = B \cdot A$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$\bar{A \cdot B} = \bar{A} + \bar{B}$$

“ Proof ”:

A	B	C	$A \cdot (B+C)$	$A \cdot B + A \cdot C$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

## BOOLEAN ALGEBRA ... continued

### *OR* rules

$$\mathbf{A + A = A}$$

$$\mathbf{A + \overline{A} = 1}$$

$$\mathbf{0 + A = A}$$

$$\mathbf{1 + A = 1}$$

$$\mathbf{A + B = B + A}$$

$$\mathbf{A + (B + C) = (A + B) + C}$$

$$\mathbf{A + B \cdot C = (A + B) \cdot (A + C)}$$

$$\mathbf{\overline{A + B} = \overline{A} \cdot \overline{B}}$$


A	B	C	$A + B \cdot C$	$(A+B) \cdot (A+C)$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

# DeMorgan's Theorem

A	B	$\overline{A \cdot B}$	$\overline{A + B}$	$\overline{\overline{A} + \overline{B}}$	$\overline{\overline{A \cdot B}}$
0	0	1	1	1	1
0	1	0	0	1	1
1	0	0	0	1	1
1	1	0	0	0	0

Diagram illustrating DeMorgan's Theorem. A rounded rectangle on the left contains two equations:  $\overline{A \cdot B} = \overline{A + B}$  (top) and  $\overline{A + B} = \overline{A \cdot B}$  (bottom). Green arrows point from these equations to the corresponding columns in the truth table. A green bracket highlights the first three columns of the table, and another green bracket highlights the last two columns.
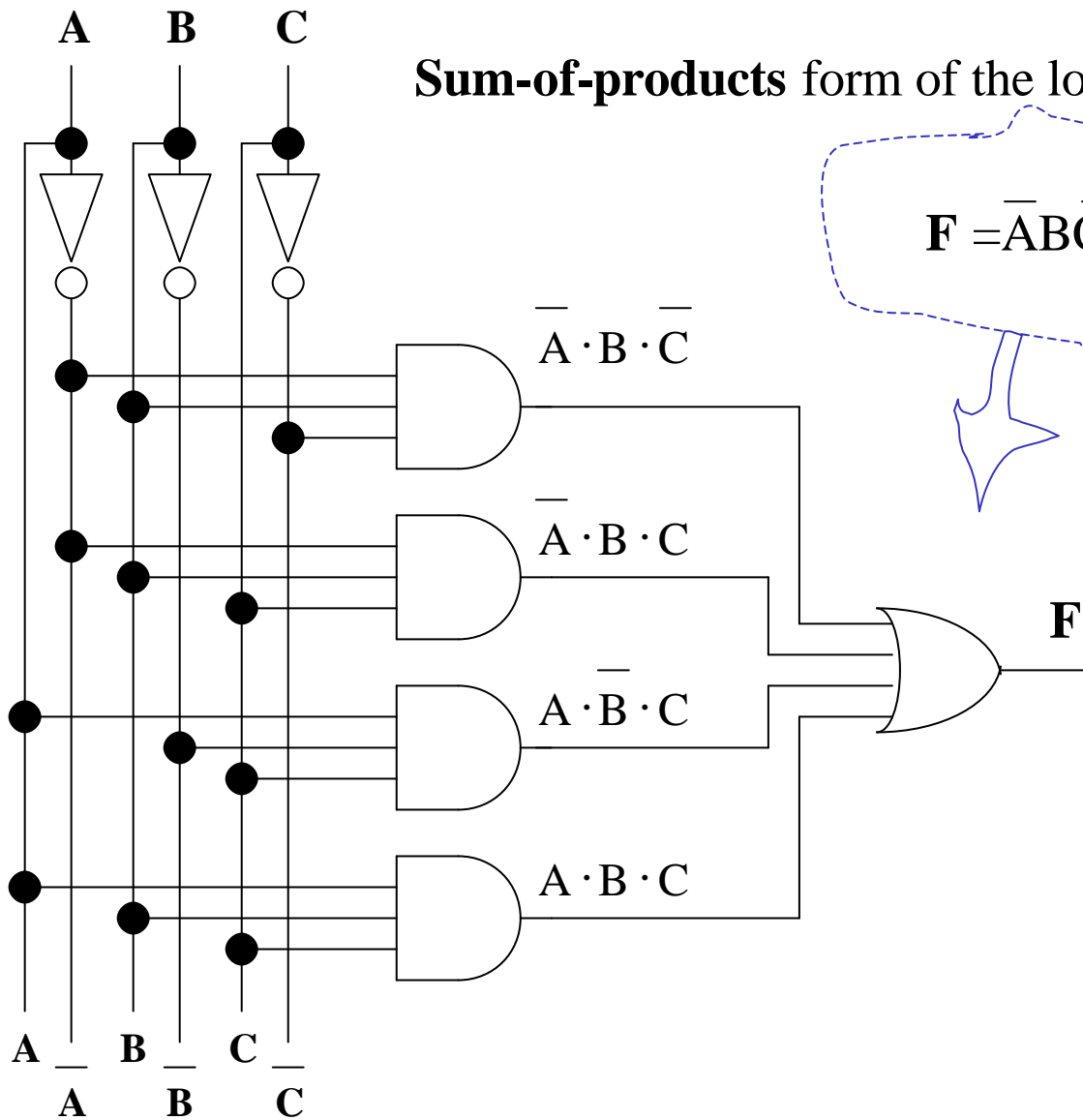
## ◆ Simplifying logic functions using Boolean algebra rules




## Simplifying logic functions using Boolean algebra rules ... continued

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

$$F = (\bar{A}\bar{B}\bar{C} + \bar{A}BC) + (A\bar{B}\bar{C} + ABC)$$

$$F = \bar{A}(B\bar{C} + BC) + A(\bar{B}\bar{C} + BC)$$
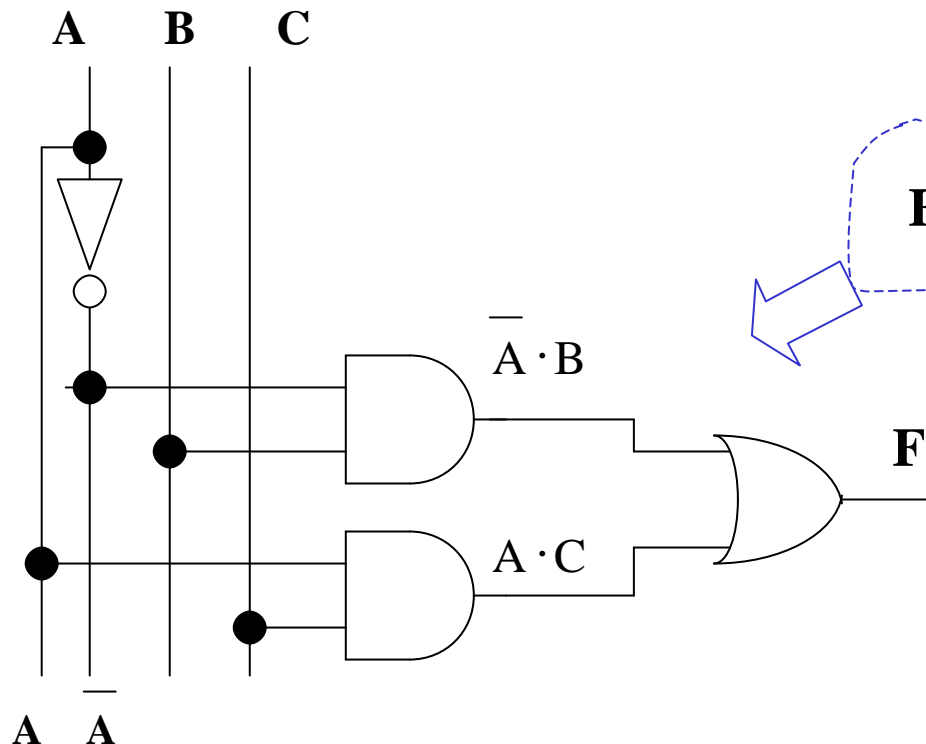
$$F = \bar{A}B(\underbrace{\bar{C} + C}_1) + AC(\underbrace{\bar{B} + B}_1)$$



## ◆ Simplifying logic functions using Karnaugh maps

★ **Karnaugh map** => graphical representation of a truth table for a logic function.

★ Each line in the truth table corresponds to a square in the Karnaugh map.

★ The Karnaugh map squares are labeled so that horizontally or vertically adjacent squares differ only in one variable. (*Each square in the top row is considered to be adjacent to a corresponding square in the bottom row. Each square in the left most column is considered to be adjacent to a corresponding square in the right most column.*)

	A	B	C	F
(0)	0	0	0	...
(1)	0	0	1	...
(2)	0	1	0	...
(3)	0	1	1	...
(4)	1	0	0	...
(5)	1	0	1	...
(6)	1	1	0	...
(7)	1	1	1	...


A B	00	01	11	10
C 0	0	2	6	4
C 1	1	3	7	5

Karnaugh map



## Simplifying logic functions of 4 variables using Karnaugh maps

	<b>A</b>	<b>B</b>	<b>C</b>	<b>D</b>	<b>F</b>
(0)	0	0	0	0	...
(1)	0	0	0	1	...
(2)	0	0	1	0	...
(3)	0	0	1	1	...
(4)	0	1	0	0	...
(5)	0	1	0	1	...
(6)	0	1	1	0	...
(7)	0	1	1	1	...
(8)	1	0	0	0	...
(9)	1	0	0	1	...
(10)	1	0	1	0	...
(11)	1	0	1	1	...
(12)	1	1	0	0	...
(13)	1	1	0	1	...
(14)	1	1	1	0	...
(15)	1	1	1	1	...

 


		<b>A B</b>			
		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>C D</b>	<b>00</b>	0	4	12	8
	<b>01</b>	1	5	13	9
	<b>11</b>	3	7	15	11
	<b>10</b>	2	6	14	10

## Simplifying logic functions using Karnaugh maps ... looping

- ★ The logic expressions for an output can be simplified by properly combining squares (**looping**) in the Karnaugh maps which contain **1s**.
- ★ Looping a pair of adjacent **1s** eliminates the variable that appears in both direct and complemented form.

	A	B	C	F
(0)	0	0	0	0
(1)	0	0	1	0
(2)	0	1	0	1
(3)	0	1	1	1
(4)	1	0	0	0
(5)	1	0	1	1
(6)	1	1	0	0
(7)	1	1	1	1

 


→  $F = \bar{A}B + AC$

## Simplifying logic functions using Karnaugh maps ... more looping

	A	B	C	D	F
(0)	0	0	0	0	1
(1)	0	0	0	1	0
(2)	0	0	1	0	1
(3)	0	0	1	1	0
(4)	0	1	0	0	0
(5)	0	1	0	1	1
(6)	0	1	1	0	0
(7)	0	1	1	1	1
(8)	1	0	0	0	0
(9)	1	0	0	1	0
(10)	1	0	1	0	0
(11)	1	0	1	1	0
(12)	1	1	0	0	1
(13)	1	1	0	1	1
(14)	1	1	1	0	1
(15)	1	1	1	1	1

 ★ Looping a *quad* of adjacent 1s eliminates the two variables that appears in both direct and complemented form.





$$F = \overline{A}\overline{B}\overline{D} + AB + BD$$

## DeMorgan's Theorem

$$\overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A + B}}$$

$$\overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}}$$


## Equivalent Gate Symbols

  
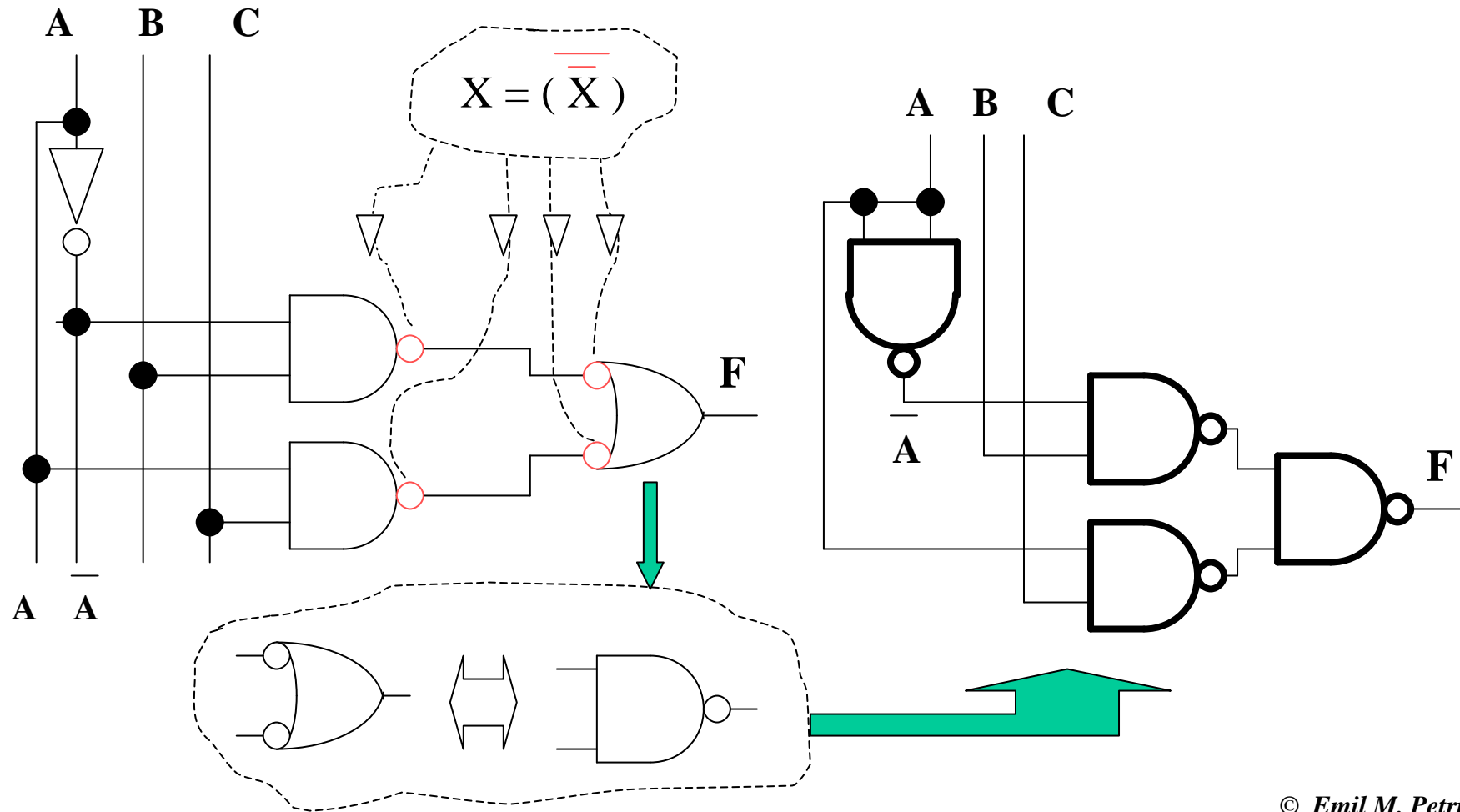
# NAND gate implementation of the “sum-of-product” logic functions

$$F = \bar{A}B + AC$$


▶ NAND gates are faster than ANDs and ORs in most technologies





# ADDING BINARY NUMBERS

◆ Adding two bits:

 

The binary number 10 is equivalent to the decimal 2


Truth table

Inputs		Outputs	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Half-Adder circuit

$Sum = A \oplus B$

$Carry = A \cdot B$


 




 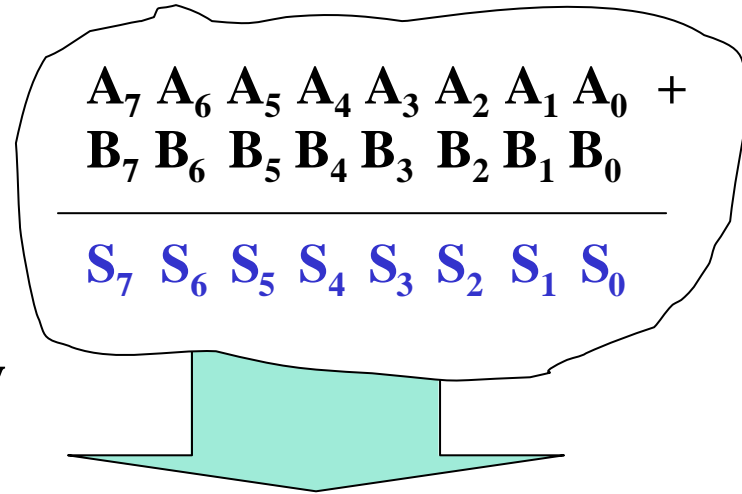
### Adding multi-bit numbers:

$$\begin{array}{r}
 108_D + \quad \rightarrow \quad 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ + \\
 90_D \quad \rightarrow \quad 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \\
 \hline
 198_D \quad \leftarrow \quad 1 \ 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \quad \leftarrow \text{Sum}
 \end{array}$$

$$\begin{array}{r}
 \quad \quad \quad \swarrow \swarrow \swarrow \swarrow \swarrow \swarrow \\
 \quad \quad \quad 0 \ 1 \ 1 \ 1 \ 1 \ 0 \ 0 \ 0 \quad \leftarrow \text{Carry}
 \end{array}$$



## ► Full Adder

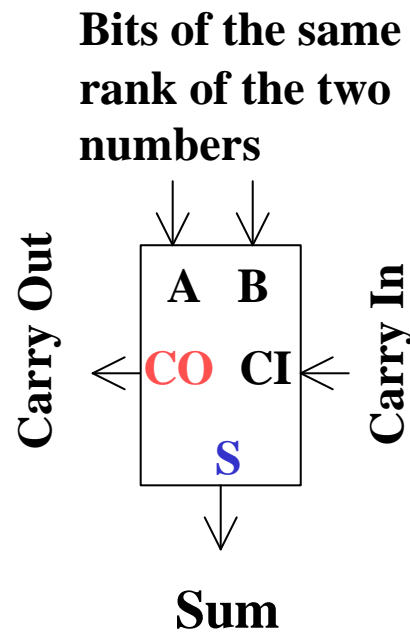

Inputs			Outputs	
A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

A B	S			
CI \	00	01	11	10
0	0	1	0	1
1	1	0	1	0

A B	CO			
CI \	00	01	11	10
0	0	0	1	0
1	0	1	1	1

A · B

B · CI

A · CI

$$S = \overline{A} \cdot \overline{B} \cdot \overline{CI} + \overline{A} \cdot \overline{B} \cdot CI + A \cdot \overline{B} \cdot \overline{CI} + A \cdot \overline{B} \cdot CI$$


$$C = A \cdot B + B \cdot CI + A \cdot CI$$





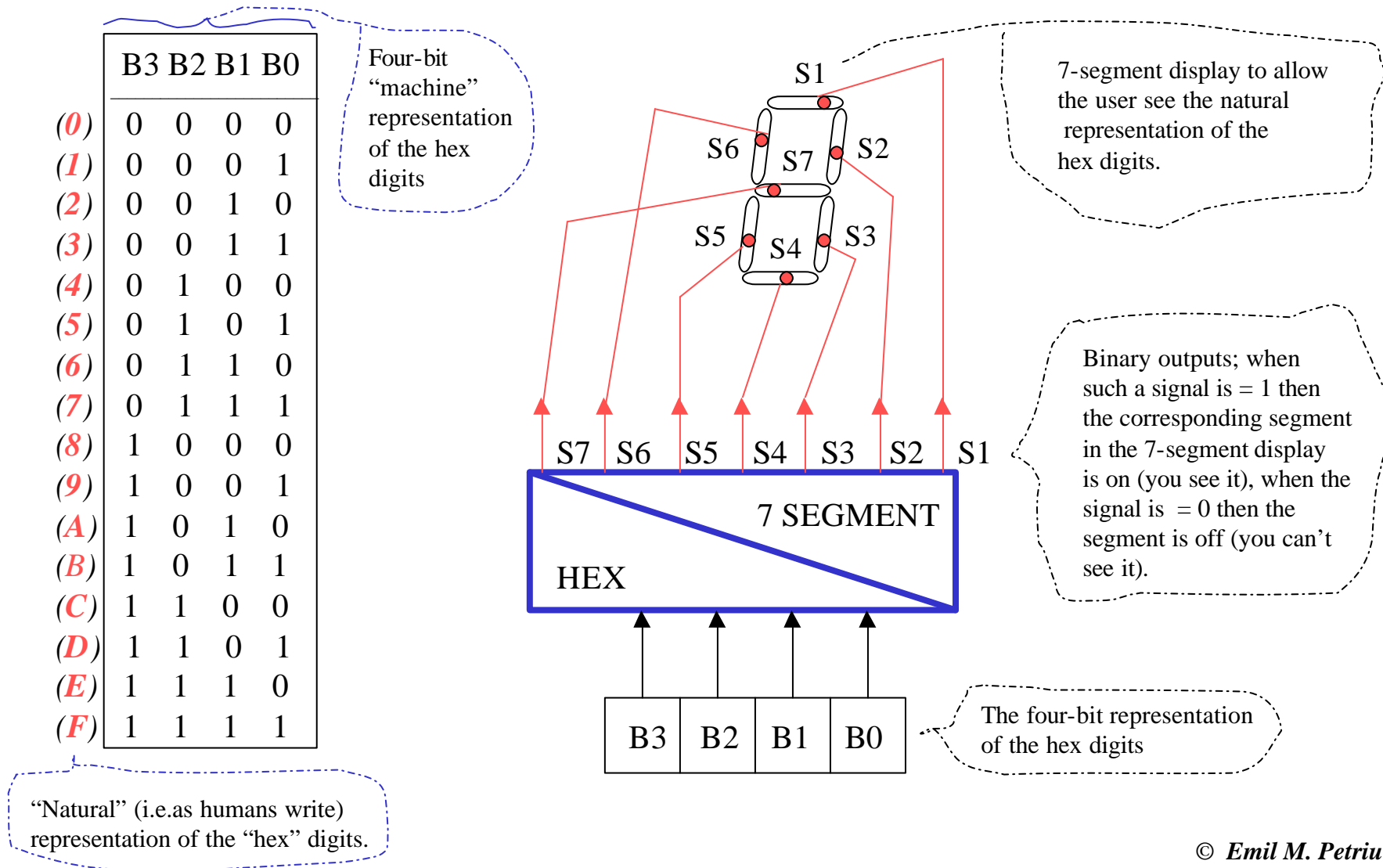
# HEX-TO-7 SEGMENT DECODER

► This examples illustrates how a practical problem is analyzed in order to generate truth tables, and then how truth table-defined functions are mapped on Karnaugh maps.



	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(A)	1	0	1	0
(B)	1	0	1	1
(C)	1	1	0	0
(D)	1	1	0	1
(E)	1	1	1	0
(F)	1	1	1	1

 

We are developing ad-hoc "binary-hex logic" expressions used just for our convenience in the problem analysis process. Each expression will enumerate only those **hex digits** when the specific display-segment is "on":



$$S1 = 0+2+3+5+6+7+8+9+A+C+E+F$$

$$S2 = 0+1+2+3+4+7+8+9+A+D$$


$$S3 = 0+1+3+4+5+6+7+8+9+A+B+D$$

$$S4 = 0+2+3+5+6+8+9+B+C+D+E$$

$$S5 = 0+2+6+8+A+B+C+D+E+F$$

$$S6 = 0+4+5+6+8+9+A+B+C+E+F$$

$$S7 = 2+3+4+5+6+8+9+A+B+D+E+F$$

 

◆ Hex-to-7 segment

	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(A)	1	0	1	0
(B)	1	0	1	1
(C)	1	1	0	0
(D)	1	1	0	1
(E)	1	1	1	0
(F)	1	1	1	1

$$S1 = 0+2+3+5+6+7+8+9+A+C+E+F$$

$$S2 = 0+1+2+3+4+7+8+9+A+D$$

$$S3 = 0+1+3+4+5+6+7+8+9+A+B+D$$

$$S4 = 0+2+3+5+6+8+9+B+C+D+E$$

$$S5 = 0+2+6+8+A+B+C+D+E+F$$

$$S6 = 0+4+5+6+8+9+A+B+C+E+F$$

$$S7 = 2+3+4+5+6+8+9+A+B+D+E+F$$

		B3 B2			
		B1 B0			
		00	01	11	10
00	0	4	C	8	
01	1	5	D	9	
11	3	7	F	B	
10	2	6	E	A	

As we are using ad-hoc “binary-hex logic” equations, (i.e. binary S... outputs as functions of hex variables) it will be useful in this case to have hex-labeled Karnaugh map, instead of the usual 2-D (i.e. two dimensional) binary labeled K maps. This will allow for a more convenient mapping of the “binary-hex” logic equations onto the K-maps.



◆ Hex-to-7 segment

Mapping the ad-hoc “binary-hex logic” equations onto Karnaugh maps:

		B3 B2			
		B1 B0	00	01	11
B3 B2	00	0	4	C	8
	01	1	5	D	9
	11	3	7	F	B
	10	2	6	E	A

$$S1 = 0+2+3+5+6+7+8+9+A+C+E+F$$

$$S2 = 0+1+2+3+4+7+8+9+A+D$$

$$S3 = 0+1+3+4+5+6+7+8+9+A+B+D$$

$$S4 = 0+2+3+5+6+8+9+B+C+D+E$$

		S1			
		B1 B0	00	01	11
B3 B2	00	1	0	1	1
	01	0	1	0	1
	11	1	1	1	0
	10	1	1	1	1

		S2			
		B1 B0	00	01	11
B3 B2	00	1	1	0	1
	01	1	0	1	1
	11	1	1	0	0
	10	1	0	0	1

		S3			
		B1 B0	00	01	11
B3 B2	00	1	1	0	1
	01	1	1	1	1
	11	1	1	0	1
	10	0	1	0	1

		S4			
		B1 B0	00	01	11
B3 B2	00	1	0	1	1
	01	0	1	1	1
	11	1	0	0	1
	10	1	1	1	0

◆ Hex-to-7 segment

B3 B2				
B1 B0	00	01	11	10
00	0	4	C	8
01	1	5	D	9
11	3	7	F	B
10	2	6	E	A

		S5			
B3 B2	B1 B0	00	01	11	10
00	1	0	1	1	
01	0	0	1	0	
11	0	0	1	1	
10	1	1	1	1	

		S6			
B3 B2	B1 B0	00	01	11	10
00	1	1	1	1	
01	0	1	0	1	
11	0	0	1	1	
10	0	1	1	1	

		S7			
B3 B2	B1 B0	00	01	11	10
00	0	1	0	1	
01	0	1	1	1	
11	1	0	1	1	
10	1	1	1	1	

$$S5 = 0 + 2 + 6 + 8 + A + B + C + D + E + F$$

$$S6 = 0 + 4 + 5 + 6 + 8 + 9 + A + B + C + E + F$$

$$S7 = 2 + 3 + 4 + 5 + 6 + 8 + 9 + A + B + D + E + F$$



# SYSTEMS of LOGIC FUNCTIONS

## ▷ 2- bit Comparator

	<b>A<sub>1</sub></b>	<b>A<sub>0</sub></b>	<b>B<sub>1</sub></b>	<b>B<sub>0</sub></b>	<b>F<sub>1</sub></b>	<b>F<sub>2</sub></b>	<b>F<sub>3</sub></b>
(0)	0	0	0	0	1	0	0
(1)	0	0	0	1	0	0	1
(2)	0	0	1	0	0	0	1
(3)	0	0	1	1	0	0	1
(4)	0	1	0	0	0	1	0
(5)	0	1	0	1	1	0	0
(6)	0	1	1	0	0	0	1
(7)	0	1	1	1	0	0	1
(8)	1	0	0	0	0	1	0
(9)	1	0	0	1	0	1	0
(10)	1	0	1	0	1	0	0
(11)	1	0	1	1	0	0	1
(12)	1	1	0	0	0	1	0
(13)	1	1	0	1	0	1	0
(14)	1	1	1	0	0	1	0
(15)	1	1	1	1	1	0	0



Compare two 2-bit numbers:

$$A=B \rightarrow F_1 = \Sigma (0,5,10,15)$$

$$A>B \rightarrow F_2 = \Sigma (4,8,9,12,13,14)$$

$$A<B \rightarrow F_3 = \Sigma (1,2,3,6,7,11)$$

## 2- bit Comparator

$A=B \rightarrow F_1 = \Sigma (0,5,10,15)$

		$A_1 A_0$			
		$B_1 B_0$			
$B_1 B_0$		00	01	11	10
00		0	4	12	8
01		1	5	13	9
11		3	7	15	11
10		2	6	14	10

		$A_1 A_0$			
		$B_1 B_0$			
$B_1 B_0$		00	01	11	10
00		1	0	0	0
01		0	1	0	0
11		0	0	1	0
10		0	0	0	1

$F_1 = 1$  when both numbers, A and B, are equal which happens when all their bits of the same order are identical, i.e.  $A_0 \bar{\bar{B}}_0$  AND  $A_1 \bar{\bar{B}}_1$

$$F_1 = (\overline{A_0 \oplus B_0}) \cdot (\overline{A_1 \oplus B_1})$$

## 2- bit Comparator

$$A < B \rightarrow F_3 = \Sigma (1, 2, 3, 6, 7, 11)$$

		$A_1 A_0$	
		00	01
$B_1 B_0$	00	0	4
	01	1	5
11	3	7	
10	2	6	
		$A_1 A_0$	
		11	10
$B_1 B_0$	00	12	8
	01	13	9
11	15	11	
10	14	10	



		$A_1 A_0$	
		00	01
$B_1 B_0$	00	0	0
	01	1	0
11	1	1	
10	1	1	
		$A_1 A_0$	
		11	10
$B_1 B_0$	00	0	0
	01	0	0
11	0	0	
10	0	0	

$$F_3 = \overline{A_0}B_1B_0 + \overline{A_1}B_1 + \overline{A_1}\overline{A_0}B_0$$



## 2- bit Comparator

$$A > B \rightarrow F_2 = \Sigma (4, 8, 9, 12, 13, 14)$$

A <sub>1</sub> A <sub>0</sub>				
B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

A <sub>1</sub> A <sub>0</sub>				
B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

$$F_2 = \overline{F_1} + \overline{F_3}$$

A <sub>1</sub> A <sub>0</sub>	$F_1 + F_3$			
B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	1	0	0	0
01	1	1	0	0
11	1	1	1	1
10	1	1	0	1

A <sub>1</sub> A <sub>0</sub>	$F_1$				A <sub>1</sub> A <sub>0</sub>	$F_3$			
B <sub>1</sub> B <sub>0</sub>	00	01	11	10	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	1	0	0	0	00	0	0	0	0
01	0	1	0	0	01	1	0	0	0
11	0	0	1	0	11	1	1	0	1
10	0	0	0	1	10	1	1	0	0


2-bit Comparator

$$F_1 = \overline{(A_0 \oplus B_0)} \cdot \overline{(A_1 \oplus B_1)}$$

$$F_2 = \overline{F_1 + F_3}$$

$$F_3 = \overline{A_0}B_1B_0 + \overline{A_1}B_1 + \overline{A_1}\overline{A_0}B_0$$

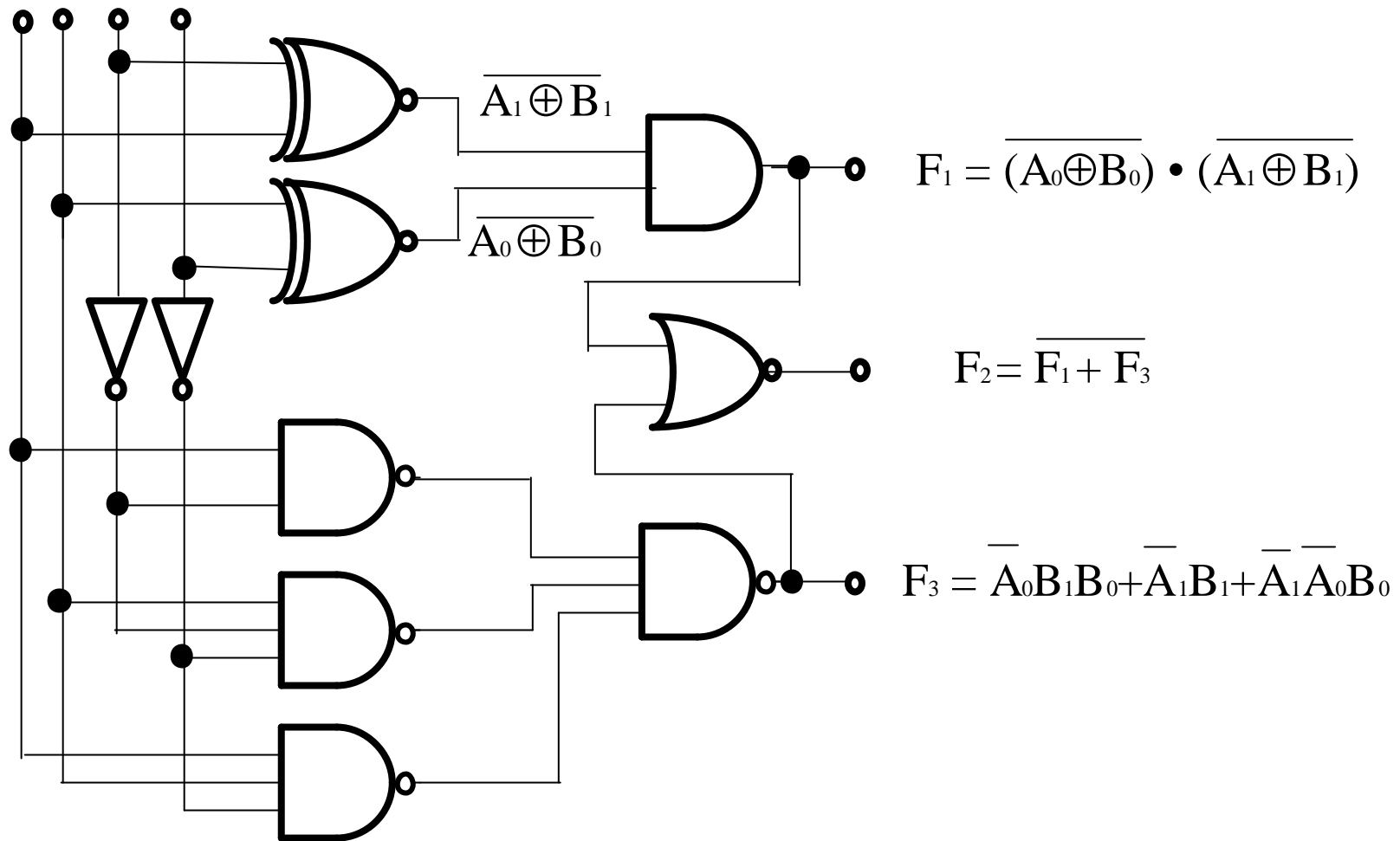
B<sub>1</sub> B<sub>0</sub> A<sub>1</sub> A<sub>0</sub>





### 3-to-8 Decoder


	A	B	C	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>
(0)	0	0	0	1	0	0	0	0	0	0	0
(1)	0	0	1	0	1	0	0	0	0	0	0
(2)	0	1	0	0	0	1	0	0	0	0	0
(3)	0	1	1	0	0	0	1	0	0	0	0
(4)	1	0	0	0	0	0	0	1	0	0	0
(5)	1	0	1	0	0	0	0	0	1	0	0
(6)	1	1	0	0	0	0	0	0	0	1	0
(7)	1	1	1	0	0	0	0	0	0	0	1

 




### 3-to-8 Decoder (74 138)

	A	B	C	$\bar{E}$	$\bar{F}_0$	$\bar{F}_1$	$\bar{F}_2$	$\bar{F}_3$	$\bar{F}_4$	$\bar{F}_5$	$\bar{F}_6$	$\bar{F}_7$
(x)	x	x	x	1	1	1	1	1	1	1	1	1
(0)	0	0	0	0	0	1	1	1	1	1	1	1
(1)	0	0	1	0	1	0	1	1	1	1	1	1
(2)	0	1	0	0	1	1	0	1	1	1	1	1
(3)	0	1	1	0	1	1	1	0	1	1	1	1
(4)	1	0	0	0	1	1	1	1	0	1	1	1
(5)	1	0	1	0	1	1	1	1	1	0	1	1
(6)	1	1	0	0	1	1	1	1	1	1	0	1
(7)	1	1	1	0	1	1	1	1	1	1	1	0

 



# BCD-TO-7 SEGMENT DECODER

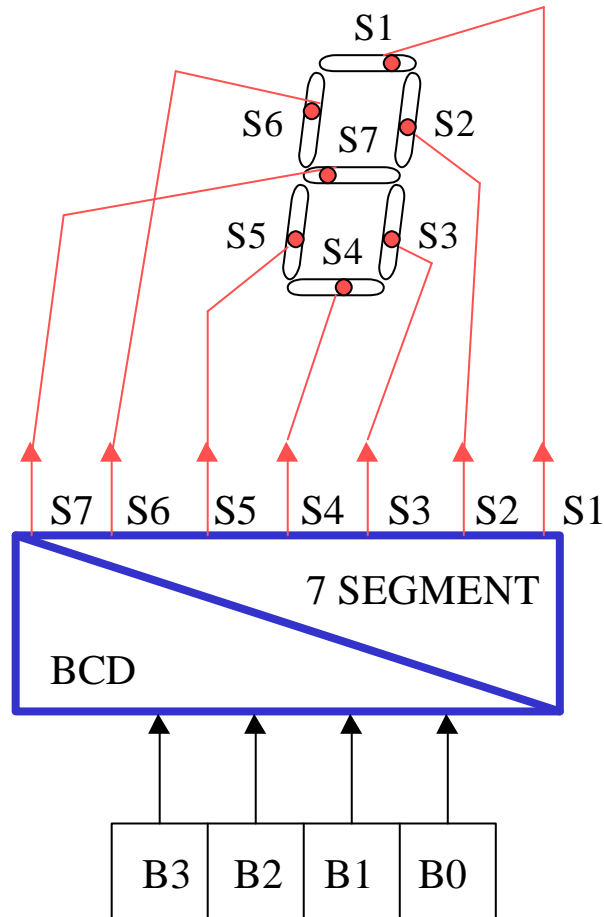


	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(x)	1	0	1	0
(x)	1	0	1	1
(x)	1	1	0	0
(x)	1	1	0	1
(x)	1	1	1	0
(x)	1	1	1	1

		B3 B2						
B1 B0	00		01		11		10	
	00	0	4	x	8			
01	1	5	x	9				
11	3	7	x	x				
10	2	6	x	x				

“Don’t Care” states/situations.  
 As it is expected that these states are never going to occur, then we may just as well use them as fill-in “1s” in a Karnaugh map if this helps to make larger loopings

◆ BCD-to-7 segment

	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(x)	1	0	1	0
(x)	1	0	1	1
(x)	1	1	0	0
(x)	1	1	0	1
(x)	1	1	1	0
(x)	1	1	1	1

 

$$S1 = 0+2+3+5+6+7+8+9$$

$$S2 = 0+1+2+3+4+7+8+9$$

$$S3 = 0+1+3+4+5+6+7+8+9$$

$$S4 = 0+2+3+5+6+8+9$$

$$S5 = 0+2+6+8$$

$$S6 = 0+4+5+6+8+9$$

$$S7 = 2+3+4+5+6+8+9$$

◆ BCD-to-7 segment

$$S1 = 0+2+3+5 \\ +6+7+8+9$$

		B3 B2		
B1 B0	00	01	11	10
00	0	4	x	8
01	1	5	x	9
11	3	7	x	x
10	2	6	x	x

		S1			
		B3 B2			
B1 B0	00	01	11	10	
00	1	0	x	1	
01	0	1	x	1	
11	1	1	x	x	
10	1	1	x	x	

$$S1 = B3 + \overline{B2B0} + B1 \\ + B2B1 + B2B0$$

$$S2 = 0+1+2+3 \\ +4+7+8+9$$

		S2			
		B3 B2			
B1 B0	00	01	11	10	
00	1	1	x	1	
01	1	0	x	1	
11	1	1	x	x	
10	1	0	x	x	

$$S2 = B3 + \overline{B2} + B1B0 + \overline{B1B0}$$

◆ BCD-to-7 segment

B3 B2 B1 B0		B3 B2			
		00	01	11	10
00	0	4	x	8	
01	1	5	x	9	
11	3	7	x	x	
10	2	6	x	x	

$$S3 = 0+1+3+4+5+6+7+8+9$$

$$S4 = 0+2+3+5+6+8+9$$

(S3)

B3 B2 B1 B0		B3 B2			
		00	01	11	10
00	1	1	x	1	
01	1	1	x	1	
11	1	1	x	x	
10	0	1	x	x	

(S4)

B3 B2 B1 B0		B3 B2			
		00	01	11	10
00	1	0	x	1	
01	0	1	x	1	
11	1	0	x	x	
10	1	1	x	x	

$$S3 = B3 + B1B0 + \bar{B1} + B2$$

$$S4 = B3 + \bar{B2}\bar{B0} + \bar{B2}B1 + B2\bar{B1}B0 + B1\bar{B0}$$



		B3 B2			
B1 B0		00	01	11	10
00		0	4	x	8
01		1	5	x	9
11		3	7	x	x
10		2	6	x	x

◆ BCD-to-7 segment

$$S7 = 2+3+4+5+6+8+9$$

		B3 B2			
B1 B0		00	01	11	10
00		0	1	x	1
01		0	1	x	1
11		1	0	x	x
10		1	1	x	x

$$S5 = 0+2+6+8$$

		B3 B2			
B1 B0		00	01	11	10
00		1	0	x	1
01		0	0	x	0
11		0	0	x	x
10		1	1	x	x

$$S5 = \overline{B2}\overline{B0} + B1\overline{B0}$$

$$S6 = 0+4+5+6+8+9$$


		B3 B2			
B1 B0		00	01	11	10
00		1	1	x	1
01		0	1	x	1
11		0	0	x	x
10		0	1	x	x

$$S6 = B3 + \overline{B1}\overline{B0} + \overline{B1}B2 + B2\overline{B0}$$


$$S7 = B3 + \overline{B2}B1 + \overline{B1}B2 + B1\overline{B0}$$


 
# MEMORY ELEMENTS: LATCHES AND FLIP-FLOPS







## R-S Latch (Reset-Set)

 


$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	$\bar{Q}$

    **Weird state**  
**Set state**  
**Reset state**  
**Hold state**



# ★ *D* (Transparent) Latch

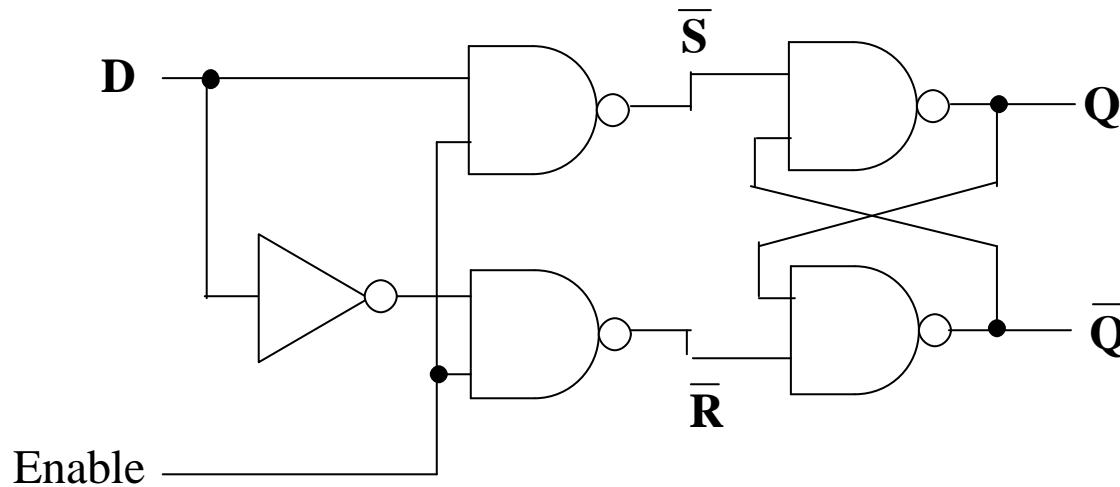

Enable	D	Q	$\bar{Q}$
0	x	Q	$\bar{Q}$
1	0	0	1
1	1	1	0


Enable	D	$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1	Q	$\bar{Q}$
0	1	1	1	Q	$\bar{Q}$
1	0	1	0	0	1
1	1	0	1	1	0


$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	$\bar{Q}$

When the *Enable* input is =1 (i.e. TRUE or HIGH) the information present at the *D* input is stored in the latch and will “appear as it is” at the *Q* output ( => it is like that there is a “transparent” path from the *D* input to the *Q* output)




◆ D Latch

 

Enable	D	$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1	Q	$\bar{Q}$
0	1	1	1	Q	$\bar{Q}$
1	0	1	0	0	1
1	1	0	1	1	0

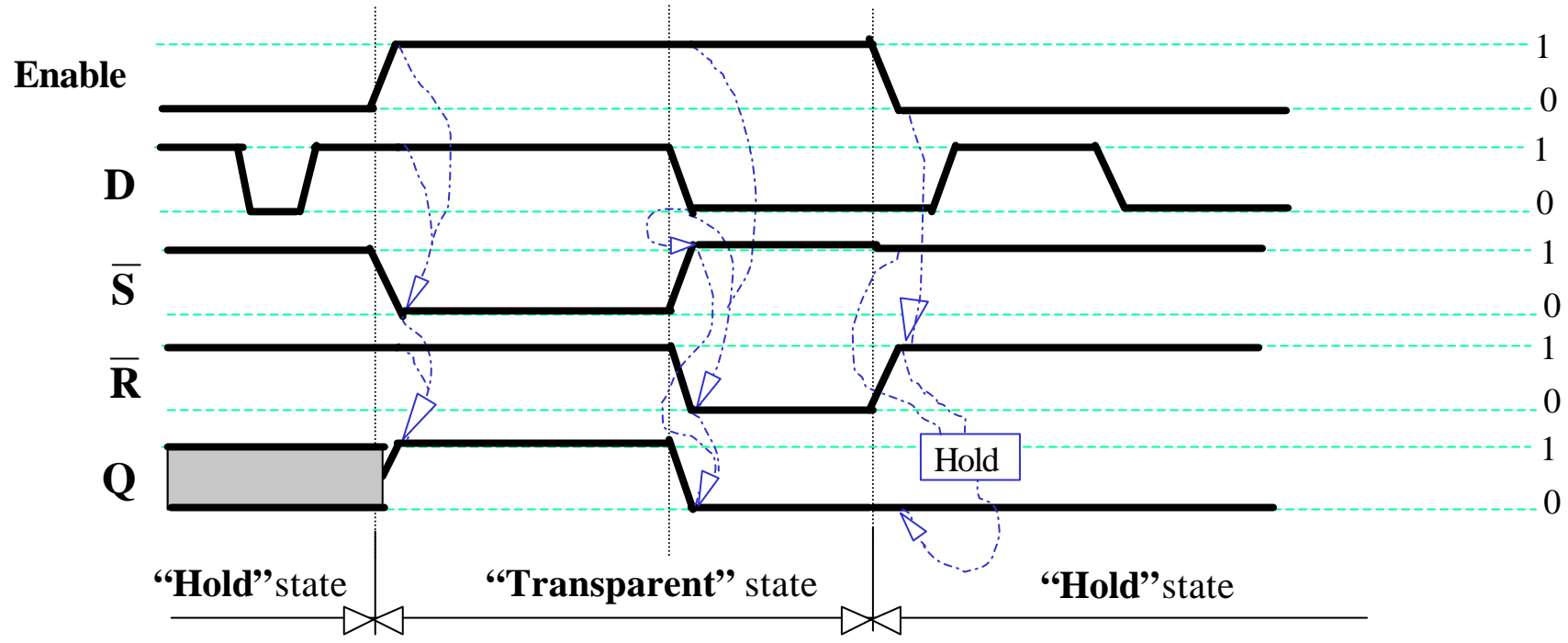


## ★ Synchronous *D* Flip-Flop

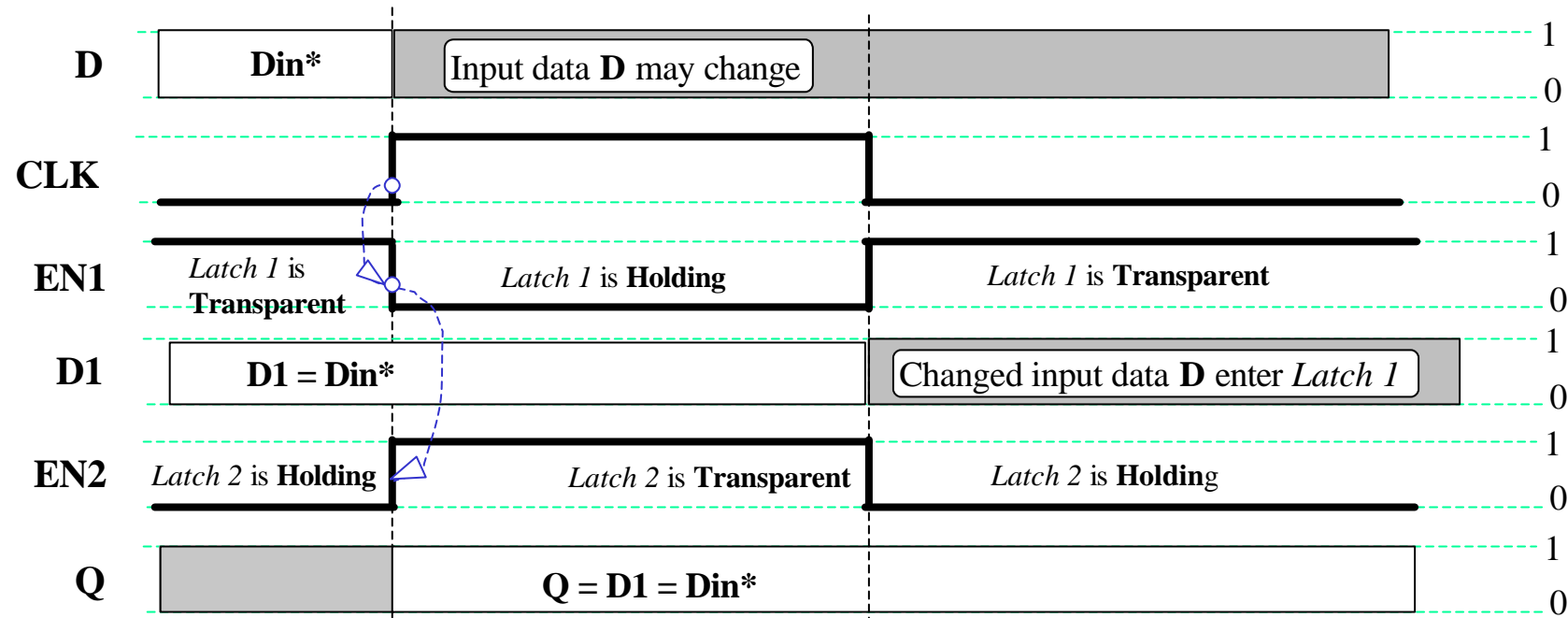 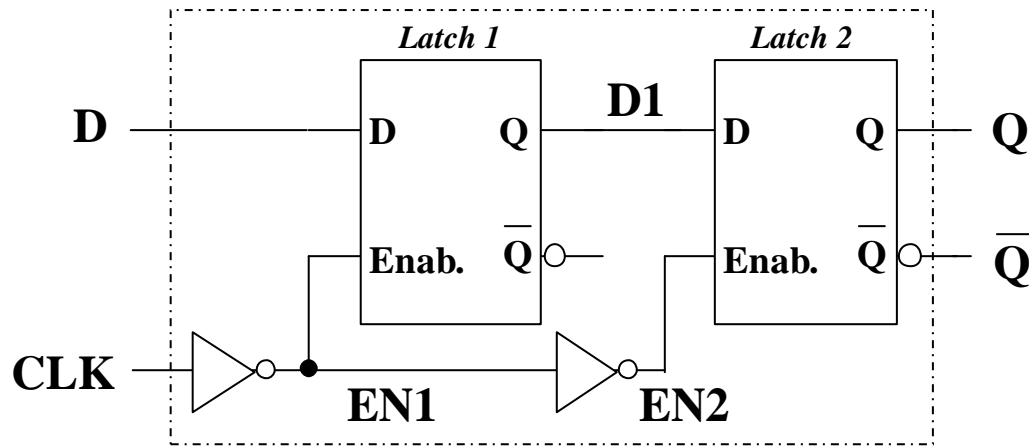

The state of the flip-flop's output **Q** copies input **D** when the positive edge of the clock **CLK** occurs

**Positive-Edge-Triggered *D* Flip-Flop**

## ◆ Synchronous D Flip-Flop

 


Connection diagram  
of the **7474 Dual  
Positive-Edge-Triggered  
D Flip-Flops** with Preset  
and Clear.





# COUNTERS
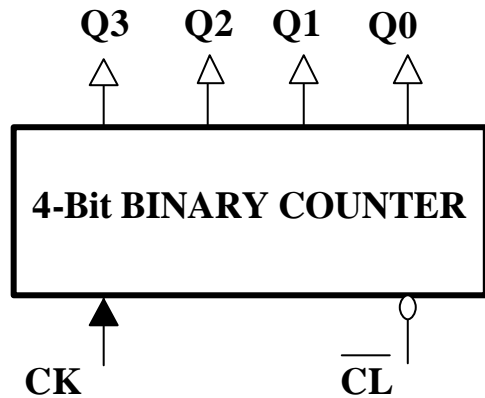
## 4-Bit Synchronous Counter using *D* Flip-Flops



$$Q = \sum_{i=0}^3 Q_i \cdot 2^i$$

  

## ◆ Synchronous 4-bit Counter

DECIMAL STATE $Q$	BINARY STATE OF THE COUNTER				FLIP FLOP INPUTS (for the next state)			
	Q3	Q2	Q1	Q0	D3	D2	D1	D0
0	0	0	0	0	0	0	0	1
1	0	0	0	1	0	0	1	0
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	1	0	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	1	0
6	0	1	1	0	0	1	1	1
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	0	1
9	1	0	0	1	1	0	1	0
10	1	0	1	0	1	0	1	1
11	1	0	1	1	1	1	0	0
12	1	1	0	0	1	1	0	1
13	1	1	0	1	1	1	1	0
14	1	1	1	0	1	1	1	1
15	1	1	1	1	0	0	0	0
0	0	0	0	0				

Using D flip-flops has the distinct advantage of a straightforward definition of the **flip-flop inputs: the current state of these inputs is the next state of the counter.** The logic equations for all four flip-flop inputs **D3, D2,**

**D1,** and **D0** are derived from this truth table as functions of the current states of the counter's flip-flops: **Q3, Q2, Q1,** and **Q0.** Karnaugh maps can be used to simplify these equations.

		Q3 Q2			
Q1 Q0		00	01	11	10
00	00	0	4	12	8
01	00	1	5	13	9
11	00	3	7	15	11
10	00	2	6	14	10

		Q3 Q2		D3	
Q1 Q0		00	01	11	10
00	00	0	0	1	1
01	00	0	0	1	1
11	00	0	1	0	1
10	00	0	0	1	1

		Q3 Q2		D2	
Q1 Q0		00	01	11	10
00	00	0	1	1	0
01	00	0	1	1	0
11	00	1	0	0	1
10	00	0	1	1	0

		Q3 Q2		D1	
Q1 Q0		00	01	11	10
00	00	0	0	0	0
01	00	1	1	1	1
11	00	0	0	0	0
10	00	1	1	1	1

		Q3 Q2		D0	
Q1 Q0		00	01	11	10
00	00	1	1	1	1
01	00	0	0	0	0
11	00	0	0	0	0
10	00	1	1	1	1



◆ Synchronous 4-bit Counter

Q3 Q2		D3			
		00	01	11	10
Q1 Q0	00	0	0	1	1
	01	0	0	1	1
	11	0	1	0	1
	10	0	0	1	1

$$D3 = Q3 \cdot \overline{Q2} + Q3 \cdot \overline{Q1} + Q3 \cdot \overline{Q0} + \overline{Q3} \cdot Q2 \cdot Q1 \cdot Q0$$

Q3 Q2		D2			
		00	01	11	10
Q1 Q0	00	0	1	1	0
	01	0	1	1	0
	11	1	0	0	1
	10	0	1	1	0

$$D2 = Q2 \cdot \overline{Q0} + Q2 \cdot \overline{Q1} + \overline{Q2} \cdot Q1 \cdot Q0$$

Q3 Q2		D1			
		00	01	11	10
Q1 Q0	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	1	1

$$D1 = \overline{Q1} \cdot Q0 + Q1 \cdot \overline{Q0}$$

Q3 Q2		D0			
		00	01	11	10
Q1 Q0	00	1	1	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	1	1

$$D0 = \overline{Q0}$$

## ◆ Synchronous 4-bit Counter

$$D_0 = \overline{Q_0}$$

$$D_1 = \overline{Q_1} \cdot Q_0 + Q_1 \cdot \overline{Q_0}$$

$$D_2 = Q_2 \cdot \overline{Q_0} + Q_2 \cdot \overline{Q_1} + \overline{Q_2} \cdot Q_1 \cdot Q_0$$

$$D_3 = Q_3 \cdot \overline{Q_2} + Q_3 \cdot \overline{Q_1} + Q_3 \cdot \overline{Q_0} \\ + \overline{Q_3} \cdot Q_2 \cdot Q_1 \cdot Q_0$$

